

Lab 3: Voltage Controlled Oscillators (VCO)

Instructor: Xiaoguang “Leo” Liu
lxgliu@ucdavis.edu
CC BY-SA 4.0

Last updated: October 26, 2018

In this lab, we will learn the techniques for characterizing high frequency voltage controlled oscillators (VCO).

1 Objectives

1. Learn how to characterize common oscillator and voltage controlled oscillator (VCO) characteristics

2 Deliverables

All items are to be submitted through Canvas.

Table 1: Lab 3 Deliverables

Item	Due date	Format	File name format
Pre-lab 3	Nov. 4th, 2018	pdf	“prelab-3-YourName.pdf”
Lab 3 report	Nov. 11th, 2018	pdf	“lab-3-GroupName.pdf”

Notes:

1. All items are due by 11:59pm of the due date. No late submissions are accepted. Don’t even ask.
2. Please follow the file name format rigorously. Replace “GroupName” with your group’s name and “YourName” with your name, first name first, last name last.

3 Prelab

1. Read the following materials:
 - EEC 134 Lecture Notes 4
 - Marc Tiebout, “VCO Basics,”
 - D. M. Pozar, “Transistor Oscillators and Frequency Synthesizers,” Chapter 8, *Microwave and RF Design of Wireless Systems*, Wiley, 2000
2. Read the Lab 3 procedures.

Pre-lab Assignment**3**

Please answer the following questions:

1. **Matching by attenuators:** A load impedance $Z_L = 5 + j200\ \Omega$ is connected to a $50\ \Omega$ system. What is the reflection coefficient at the load? If a 3 dB attenuator is connected in front of Z_L , what is the reflection coefficient seen into the attenuator? What if a 6 dB attenuator is used instead?
2. What is the pushing performance of the ADI HMC384 VCO?
3. What is the tuning sensitivity of the Maxim MAX2750 VCO?
4. Compare the phase noise performance of the Crystek CVCO55BE-2300-2500 and the Mini-Circuits ROS-2490C+ VCOs for frequency offset range of 1 kHz–1 MHz.
5. Identify the PLL loop filter (low-pass filter) circuit in the ADI ADF4159 evaluation board (EV-ADF4159EB1Z/EV-ADF4159EB3Z) schematic (Page 11–14 of the evaluation board datasheet). Redesign the loop filter for 100 kHz bandwidth and provide the filter component values.

4 Equipment & Supplies

- 1 \times GSP-730 spectrum analyzer;
- 2 \times TPI synthesizer;
- 1 \times Mini-Circuits ZX95-2536C+ VCO;
- 1 \times Mini-Circuits VAT-3+ 3 dB attenuator;
- 2 \times 12" and 2 \times 6" SMA cables;
- 1 \times USB battery pack;
- Voltage regulator circuits from Lab 1;
- Function generator circuit from Lab 1.

5 Procedures**5.1 VCO tuning characteristics**

1. Connect the 3 dB attenuator to the VCO output. Then connect the other end of the attenuator to the spectrum analyzer through an SMA cable.
2. Connect the output of your Lab 1 function generator output to the Vtune terminal of the VCO. Modify the code to allow the function generator to output a constant voltage. Set the voltage to 0 V.
3. Power up the VCO:
 - (a) Connect the voltage regulator to the Power terminal of the VCO;
 - (b) Ground the GND terminal of the VCO;

- (c) Set the breadboard voltage regulator output to 5 V; power up the voltage regulator by turning on the battery packs.

Note: We power up the VCO after we connect the output because we want to make sure that the VCO circuit sees a typical $50\ \Omega$ load condition when it powers up.

4. Turn on the spectrum analyzer. Set appropriate measurement parameters.
5. Use a multimeter to monitor the voltage on the Vtune terminal. It should read 0 at this point.
6. Adjust the function generator to set the Vtune voltage from 0 V to 5 V. Record the output frequency and power at each Vtune. You should include at least 8 data points.
7. Plot the output frequency and output power with respect to Vtune. Make sure you properly take the loss of the attenuator and the cable into account.
8. Compare your measurement result with the VCO's datasheet.
9. Do a linear fit of the VCO frequency tuning characteristics. How good is this fit? Discuss your result.
10. **Challenge!** If you use the triangle wave output of your function generator, the output frequency of the VCO will not be a linear function with respect to time. Could you modify the function generator output to compensate for this non-linearity?
11. Do not disassemble the setup at the end of this lab.

5.2 VCO pushing characteristics

1. With the same setup as in Experiment 5.1, set VTUNE to any constant value between 0 V and 5 V.
2. Adjust the VCO supply voltage using the potentiometer in your voltage regulator circuit from 5 V to 4 V. Record the VCO output frequency and power at each supply voltage. You should include at least 8 data points.
3. Plot the output frequency and output power with respect to Vcc. Make sure you properly take the loss of the attenuator and the cable into account. Compare your measurement result with the VCO's datasheet.