

Lab 2: Characterization of RF Amplifiers

Instructor: Xiaoguang “Leo” Liu

lxgliu@ucdavis.edu

CC BY-SA 4.0

The second lab revolves around the most common component in a high frequency electronic system, the RF amplifier. RF amplifiers are used to amplify weak RF signals for either transmission or detection. They are designed differently depending on where they are used in the system. For example, low noise amplifiers (LNA) are usually used as the first stage of a receiver to minimize system noise; they are usually designed for the lowest noise possible, sometimes even at the sacrifice of gain and efficiency. On the other hand, a power amplifier is usually the last stage before the antenna in a transmitter; they are usually designed to generate the highest amount of power possible while maintaining decent power efficiency and linearity; noise performance is less of a concern because the transmitted signal is usually quite strong. Regardless of how they are designed, RF amplifiers share similar performance metrics, such as noise, linearity, power handling, and power efficiency. In this lab, we will learn and practice techniques for characterizing RF amplifiers.

1 Objectives

1. Learn the basic operations of an RF spectrum analyzer;
2. Understand major RF amplifier performance metrics, including bandwidth, noise figure, gain, compression, and intermodulation;
3. Learn the experimental techniques for characterizing the above metrics;
4. Learn the basics of RF PCB design.

2 Deliverables

All items are to be submitted to the TA's email: eec134f2016@gmail.com.

Table 1: Lab 2 Deliverables

Item	Due date	Format	File name format
Pre-lab 2.1	Oct. 20th, 2016	pdf	"prelab-2-1-YourName.pdf"
Pre-lab 2.2	Oct. 27th, 2016	pdf	"prelab-2-2-YourName.pdf"
Lab 2 report	Nov. 3rd, 2015	pdf	"lab-2-GroupName.pdf"
PCB 2 design & review reports	Nov. 3rd, 2016	pdf	"pcb-2-report-GroupName.pdf"
PCB 2 gerber files	Nov. 3rd, 2016	zip	"pcb-2-design-GroupName.zip"
PCB 2 test report	Nov. 24th, 2016	pdf	"pcb-2-test-GroupName.pdf"
PCB 3 design & review reports	Nov. 10th, 2016	pdf	"pcb-3-report-GroupName.pdf"
PCB 3 gerber files	Nov. 10th, 2016	zip	"pcb-3-design-GroupName.zip"
PCB 3 test report	Dec. 1st, 2016	pdf	"pcb-3-test-GroupName.pdf"

Notes:

1. All items are due by noon (12pm) of the due date. No late submissions are accepted. Don't even ask.
2. Please follow the file name format rigorously. Replace "GroupName" with your group's name and "YourName" with your name, first name first, last name last.

3 Prelab

3.1 A simplistic introduction to spectrum analyzers

In EEC134, we are going to use a spectrum analyzer as the main RF measurement tool. A beard well lathered is half shaved; before we start the actual labs, let's learn a little bit about spectrum analyzers.

A spectrum analyzer is a very useful and versatile instrument for characterizing high frequency signals, circuits, and systems. In its basic form, a spectrum analyzer measures the average power of the signals that come into its input port with respect to frequency. Fig. 1 shows a conceptual comparison between an oscilloscope and a spectrum analyzer. While an oscilloscope displays the input signal in the time domain, a spectrum analyzer displays the signal in the frequency domain¹.

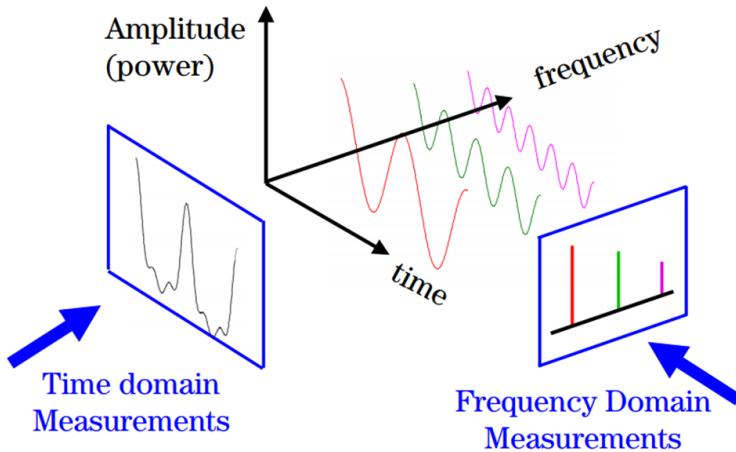


Figure 1: Conceptual comparison between time domain measurements (oscilloscope) and frequency domain measurements (spectrum analyzer) [1]

Fig. 2 shows a screen capture of a typical spectrum analyzer measurement. The horizontal axis is frequency and the vertical axis is signal power in dB scale. This figure shows a fairly narrow band signal at 1.8271 GHz. The power of the signal is 2.06 dBm.

At other frequencies where there is no input signal, we can still observe some measurement. As you might have guessed, these signals represent the noise, both from the signal source and from the spectrum analyzer itself. Obviously, it is important to have as low of a noise level as possible in order to detect extremely weak input signals. In fact, an important metric of a spectrum analyzer's performance is its sensitivity, i.e. the weakest signal that it can measure. This is often specified as *Displayed Average Noise Level* (DANL), usually measured in dBm at the smallest *resolution bandwidth*

¹Todays high end oscilloscopes and spectrum analyzers have become so complex that their distinction is becoming ambiguous: oscilloscopes may now have built-in frequency analysis tools such a Fourier Transform processing engine; spectrum analyzers may now have enough memory to store and display the signals spectrum variations with respect to time.

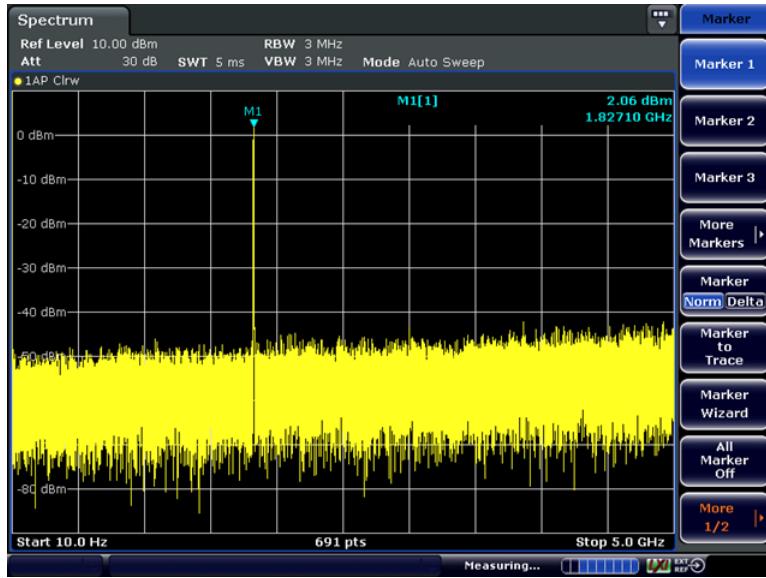


Figure 2: Simplified block diagram of a spectrum analyzer.

(RBW, we will come to this soon), or directly in dBm/Hz. The sensitivity is then simply DANL+SNR, where SNR is the minimum required *signal to noise ratio*. For a top of the line spectrum analyzer, you can expect a DANL of close to -170 dBm/Hz.

Another related metric is the *dynamic range*, which refers to the power difference between the strongest and the weakest signal a spectrum analyzer can measure. Dynamic range is usually specified in dB. The absolute maximum dynamic range that a spectrum analyzer can achieve is the difference between the maximum allowable input power and the DANL. Sensitivity and dynamic range speak for the design and build quality of a spectrum analyzer. However, the achievable sensitivity and dynamic range in an actual measurement are usually lower than the maximum. It depends on what you want to measure and how you set up the spectrum analyzer. To understand this, we need to learn a bit more about how a spectrum analyzer works.

The basic working principle of a typical spectrum analyzer is conceptually quite simple². It is basically a glorified high frequency signal receiver. Fig. 3 shows a very simplified system diagram of a typical spectrum analyzer, highlighting its major blocks. The input signal is downconverted to a much lower frequency (usually several MHz) before it is captured by a power detector. The downconverter is represented by a mixer with a sweeping local oscillator (LO). The LO signal is swept through a span of frequency that can be set by the user; this sets the frequency span of the measurement. The downconversion of the signal allows it to be optimally conditioned for the detection circuitry.

Before the downconverted signal enters the power detector, a narrow-band

²The actual implementation of an instrument grade spectrum analyzer can be extremely complex to meet the high performance specs

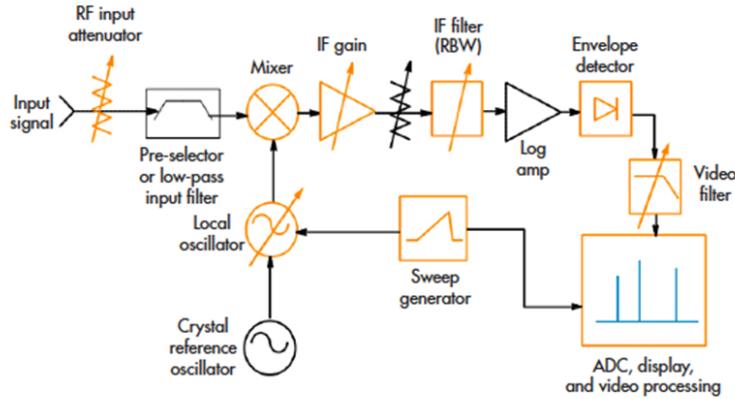


Figure 3: Simplified block diagram of a spectrum analyzer [2].

filter is used to allow only the desired signal to pass. This filter not only eliminates spurious signals but also limits the amount of noise power that enters the detector. As you can imagine, the narrower the filter passband is, the lower the noise floor would be. This filter is called the IF filter, and its bandwidth is called the resolution bandwidth (RBW). The power detector is effectively detecting the total power (signal plus noise) inside the resolution bandwidth. The best sensitivity and dynamic range of a spectrum analyzer can only be achieved with the narrowest RBW that is available in the instrument. Therefore, the available RBW bandwidth becomes an important metric itself.

Besides affecting the noise floor, the RBW also has implications on how the signal looks on the screen. Consider the case of an ideal single-tone (meaning single frequency) input signal. The spectrum of this signal should look like a delta function in the frequency domain. Now imagine the receiver of the spectrum analyzer sweeps through the center frequency of the signal. Due to the finite width of the RBW, the measured spectrum will actually take the shape of the RBW filter! By carefully taking into the account of the RBW filter frequency response, the measured signal power and frequency can still be reconstructed. However, you would not be so lucky if you are dealing with more than one signal. Fig. 4 shows a scenario where three closely located signals cannot be reliably discerned by a large RBW.

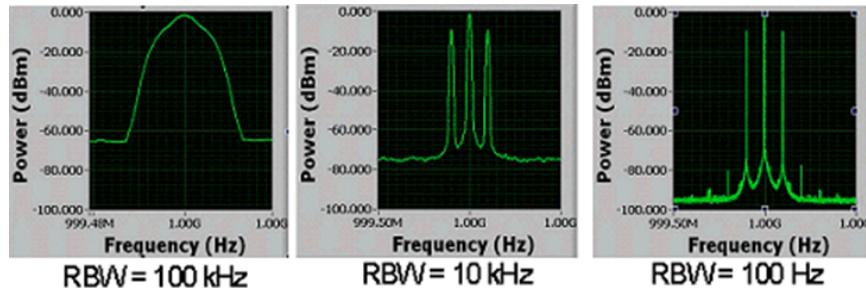


Figure 4: Small RBW resolves closely located signals.

It becomes clear that an infinitely narrow IF filter is needed to faithfully reconstruct the true spectrum of the input signal. Obviously such a filter does not exist, and you will always have to keep in mind the broadening of the spectrum in a spectrum analyzer measurement.

This simplistic introduction to spectrum analyzers will end here. There is obviously much more to learn about this fundamental high frequency signal characterization tool. To get a deeper understanding of spectrum analyzers and the principles of spectrum analysis, the following documents are recommended as further reading materials.

- “Spectrum analysis basics,” Agilent application note AN-150.
- “Fundamentals of Real-Time Spectrum Analysis,” Tektronix application note.
- Rigol DSA1030A-TG3 spectrum analyzer review and experiments (Video³):
<https://www.youtube.com/watch?v=lu2Uaj3ZcoA>

3.2 Coaxial RF Connectors

As we learned in the introductory engineering electromagnetics course, electrical connections between high frequency circuit components may not be as simple as in the case of low frequency circuits. We have to consider wave propagation effects (transmission line effects) when the length of the connection is comparable with the wavelength. As a consequence, we have to consider impedance matching between the transmission lines and the circuit components. To make things simple, we often conform to a single impedance value, often called the system impedance, in an RF system. In most systems, this impedance value is $50\Omega^4$.

Perhaps the most prevalent transmission line for medium to low-power RF/microwave systems is the coaxial cable, which consists of an inner conductor and an outer conductor arranged in a cylindrical fashion. Coaxial cables are great because they are generally low loss, can be made flexible, and provide great shielding/isolation of the signal being transmitted. In order to connect coaxial cables to an RF block, a coaxial RF connector is usually used.

RF connectors comes in many different standards. They vary in shape, usable frequency range, signal attenuation, power handling, durability, etc. Fig. 5 provides a glimpse of some common RF connectors.

To learn about RF coaxial connectors, go through the following materials.

- “Guidance Selecting Handling Coaxial RF Connectors,” Rohde & Schwarz.

³This Youtube channel features many great tutorial videos related to high frequency electronics.

⁴Why 50 ? read the following: <http://www.belden.com/blog/broadcastav/50-ohms-the-forgotten-impedance.cfm>



Figure 5: Typical RF connectors. Source: http://www.szelins.com/RF_Connector.html

**Pre-lab Assignment
2.1**

Due: Oct. 20th, 2016

Please review EEC134 Lecture Note 3 and answer the following questions:

- a) A 10 dBm 2.4 GHz RF signal is sent through a 50Ω TEM transmission line to a 50Ω load. Assuming that the source impedance is also 50Ω , what is the RMS voltage on the transmission line (i.e. between the transmission line's signal and ground)?
- b) An RF signal of 0 dBm power is amplified by an amplifier with 14 dB power gain. The source impedance of the input signal is 50Ω and is well matched with the input impedance of the amplifier. The output of the impedance of the amplifier is 200Ω and is also well matched with a 200Ω load. What's the voltage swing at the output of the amplifier?
- c) A transmission line of characteristic impedance Z_t and length l is connected to a load impedance of Z_0 . What is the reflection coefficient at the input of the transmission line for the following conditions? What observation can you make?
 - i) $Z_t = 5Z_0$, $l = 0.5\lambda$;
 - ii) $Z_t = 5Z_0$, $l = 0.25\lambda$;
 - iii) $Z_t = 5Z_0$, $l = 0.1\lambda$;
 - iv) $Z_t = 5Z_0$, $l = 0.05\lambda$;
 - v) $Z_t = 5Z_0$, $l = 0.01\lambda$;
 - vi) $Z_t = 0.2Z_0$, $l = 0.5\lambda$;
 - vii) $Z_t = 0.2Z_0$, $l = 0.25\lambda$;
 - viii) $Z_t = 0.2Z_0$, $l = 0.1\lambda$;

- ix) $Z_t = 0.2Z_0, l = 0.05\lambda;$
 x) $Z_t = 0.2Z_0, l = 0.01\lambda;$
- d) A signal is sampled at frequency F_s (in unit of samples per second). N samples have been collected. When an FFT is performed on the samples, what is the resulting frequency resolution?
- e) An RF amplifier has a noise figure of 2 dB. If an input signal with a signal to noise ratio (SNR) of 20 dB is fed into the amplifier, what is the SNR of the output signal?
- f) What connectors are mechanically compatible with the 3.5 mm type connectors? Which of these connectors has the largest operating frequency range?

Pre-lab Assignment**2.2**

Due: Oct. 27th, 2016

Please answer the following questions:

- a) Two RF amplifiers are cascaded as shown in Fig. 6. What is the total gain of the cascade? What is the total noise figure?

$$\begin{array}{ll} G_1 = 14.5 \text{ dB} & G_2 = 18.10 \text{ dB} \\ NF_1 = 0.75 \text{ dB} & NF_2 = 2.30 \text{ dB} \end{array}$$

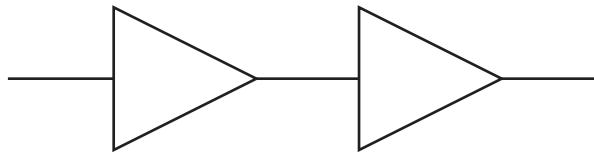


Figure 6: A cascade of two RF amplifiers.

- b) An RF amplifier has an input-output voltage relationship of the following:

$$v_o = 10v_i + 0.2v_i^2 - 0.05v_i^3,$$

where v_o is the output voltage and v_i is the input voltage. Assume that the amplifier is well matched at the input and output to 50Ω loads.

- i) Calculate the output 1 dB compression point P1dB;
 - ii) Calculate the output 3rd order intercept point OIP3;
 - iii) Calculate the output 2nd order intercept point OIP2.
- c) The Y-factor method is used to measure the equivalent noise temperature of a component, with a hot load of $T_1 = 320\text{ K}$ and cold load of $T_2 = 77\text{ K}$. If the Y-factor ratio is measured to be 0.608 dB, what is the noise figure of the component under test?
- d) What is the typical input IP3 of the Mini-Circuits GALI-84+ amplifier at 2 GHz?
- e) What is the lowest noise figure 2.4 GHz SMD RF amplifier you could find?

4 Equipment & Supplies

- 2 × Mini-Circuits ZX60-272LN-S+ amplifier (Fig. 7). Table shows its main specifications (typical values) at room temperature. More detailed specifications can be found in the datasheet (<http://www.minicircuits.com/pdfs/ZX60-272LN+.pdf>⁵).

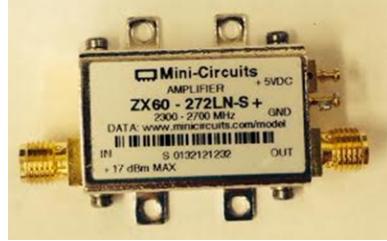


Figure 7: Picture of the Mini-Circuits ZX60-272LN-S+ amplifier.

Table 2: ZX60-272LN-S+ Typical Specifications.

Frequency range	2300 – 2700 MHz
Noise figure	0.8 dB
Gain	14 dB
P1dB	18.5 dBm
OIP3	31.5 dBm
Input VSWR	1.2
Supply voltage	5 V
Supply current	55 mA

- 1 × Mini-Circuit ZX10-2-332-S+ power splitter/combiner. An RF power splitter is used to evenly split the RF power from the input port (marked “S”) into two output ports (marked “1” and “2”). However, here we will use it as a power combiner⁶, which combine the signals from two output ports into the input port.
- 1 × Mini-Circuits VAT-3+ 3 dB RF attenuator. As its name suggests, the attenuator attenuates the RF signal by 3 dB.
- GW-Instek GSP-730 spectrum analyzer (Fig. 9). The GSP-730 is a low-cost 3 GHz spectrum analyzer. It doesn't have the best performance ⁷, but we will work around the limitations to make it useful for our labs. The GSP-730 can be remotely controlled from the lab computer by the GGT software provided by GW-Instek.

⁵It is always a good idea to read the datasheet before using a component.

⁶You will learn in an RF circuit design class that most passive RF components — splitter is one of them — are reciprocal, meaning that you use their output as input and vice versa.

⁷We've chosen this spectrum analyzer primarily for cost reasons.



Figure 8: Picture of the Mini-Circuits ZX10-2-332-S+ amplifier.

The spectrum analyzers are usually locked in the Kemper 2112 cabinet. However, your group can check one out if you wish to use it outside of lab hours. The GSP730 will fit in your EEC134 toolbox.



Figure 9: Picture of the Instek GSP730 spectrum analyzer.

- 2 × TPI synthesizers (Fig. 10) and 2 × USB-mini cables. The TPI synthesizer is a low-cost RF signal generator based on the Analog Devices AD4351 single-chip synthesizer. The synthesizers will be distributed to each group and it will be your responsibility to keep them safe.

Note that every TPI synthesizer is calibrated and has its individual serial number. When you connect the synthesizer to a computer through the USB-mini cable, a window will pop up to let you select the calibration file based on the serial number.

- 2 × 12" and 2 × 6" semi-flex coaxial SMA cables. The coaxial cables can be bent to a certain extent, but please do not bend them excessively.
- 1 × TNC (male) to SMA (female) connector.

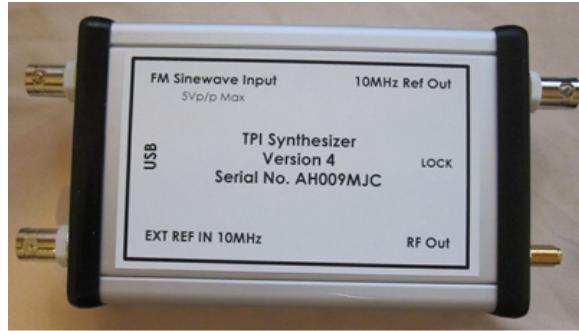


Figure 10: Picture of the TPI v4 RF synthesizer.



Figure 11: Picture of the semi-flex coaxial cable.

5 Procedures

5.1 Getting to know your equipment

In this lab, we will measure the frequency and power of an RF signal generated by the TPI synthesizer with the GSP-730 spectrum analyzer. The measurement set up is shown in Fig. 13.

1. Connect the TNC-male to SMA-female adapter to the input port of spectrum analyzer (labeled “RF INPUT 50Ω ”). Follow proper handling guidelines (in this case, hold the SMA-female end still and rotate only the TNC jacket). The adapter should be left on the spectrum analyzer from now on.
2. Connect the output of the TPI synthesizer to the input of the spectrum analyzer (with the adapter already connected) using an SMA cable.
3. Connect the TPI synthesizer to the lab computer using an USB cable (provided with the kit).
4. Turn on the spectrum analyzer and configure it as below.
 - (a) Press the “Preset” button. **Always** preset the spectrum analyzer before starting a new experiment.
 - (b) Set the center frequency. Press the blue “Frequency” button, then press the “F1” button to select the “Center” frequency option.



Figure 12: Picture of the TNC (male) to SMA (female) connector.

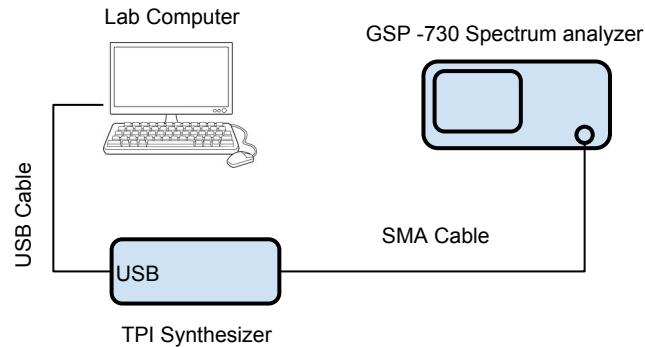


Figure 13: Testing the TPI synthesizer and the GSP-730 spectrum analyzer.

Type in “2.4 GHz” using the numerical panel on the spectrum analyzer.

- (c) Set the frequency span. Press the blue “Span” button, then press “F1” button to select the “Span” option. Type in “20 MHz”. Now you should be able to observe the frequency range from 2.39 GHz to 2.41 GHz⁸.
- (d) Set the reference level. Press the “Amplitude” button, then press “F1” button to select the “Ref. Level” option. Type in “20 dB” to set the reference level to 20 dBm⁹. The screen of the spectrum analyzer should look like that in Fig. 14.

5. Measuring a single-tone RF signal

- (a) Launch the *SynthMachine* software and choose the appropriate calibration file (serial number) for the TPI synthesizers. In the *SynthMachine* software, set the “Center Frequency” to 2400MHz , set the “Output Power” to 10 dBm, and click “RF On” to turn on the RF signal output.
- (b) Observe the spectrum analyzer screen. It should look like the following.

⁸You can also achieve this by setting the “Start frequency” and “Stop frequency”; play with it.

⁹The reference level is set to be comparable to the signal input power.

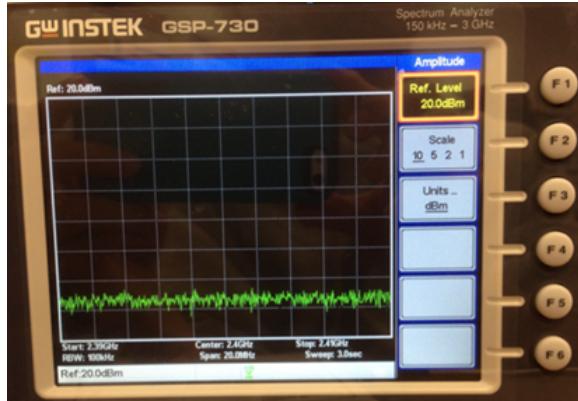


Figure 14: Setting the reference level.

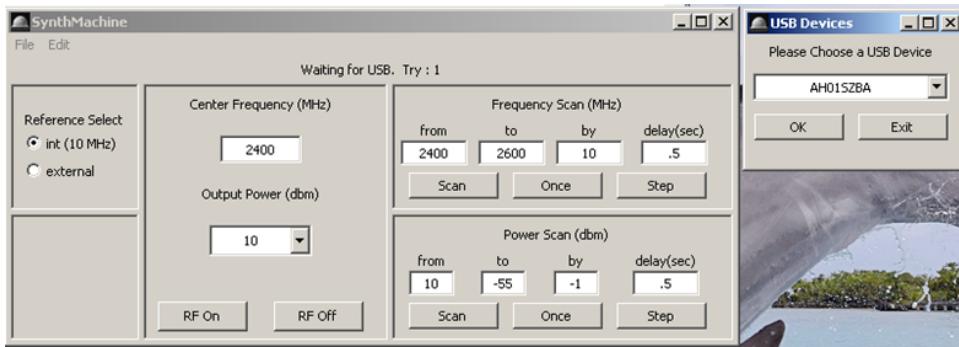


Figure 15: Screenshot of the SynthMachine software.

- (c) Press the gray “BW” (meaning bandwidth) button to go into the resolution bandwidth menu. Press “F1” to set the RBW to manual mode. Three possible RBW options should now appear in the sidebar menu. Capture the screen for each of the three settings¹⁰. In your lab report, describe the differences between the three screen captures and explain why such differences exist.
- (d) Set the RBW to the smallest possible value.
- (e) Press the “Peak Search” button, and a marker is automatically located at the RF signals. You can read the frequency and power values of this marker at the right upper corner of the screen. Record the power of this signal. How does it compare it with the output setting of the TPI synthesizer? Assume that the TPI synthesizer output power is accurate, what do you think is the cause of the difference? This measured signal power which we will designate as P_{cal} will be used as a reference for later labs.

6. Observing the harmonics.

¹⁰You can capture the screen by a camera or using the remote control software GGT. The software can be launched from the Start Menu of the lab computer. We'll leave it to you to explore how to capture the screen using the software.

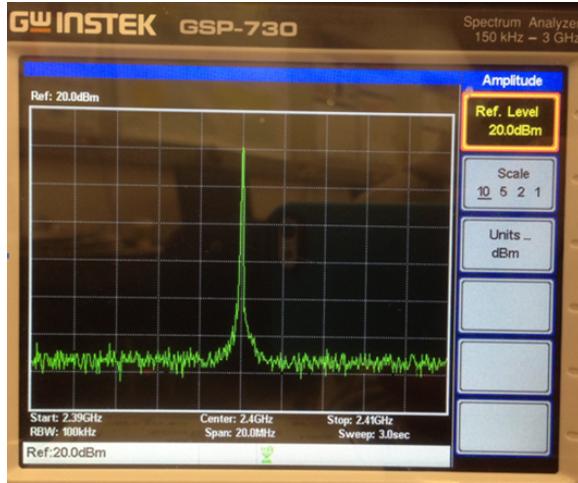


Figure 16: Screenshot of the spectrum analyzer with a single-tone input.

- (a) Now set the output frequency of the TPI synthesizer to 800 MHz.
- (b) Preset and configure the spectrum analyzer as follows:
 - i. Start frequency = 500 MHz;
 - ii. Stop frequency = 3000 MHz;
 - iii. RBW = auto;
 - iv. Reference level = 20 dBm.
7. Measuring two RF signals.
 - (a) Turn off the RF power from the TPI synthesizer.
 - (b) Disconnect the TPI synthesizer from the SMA cable.
 - (c) Connect the input port (labeled “S”) of the splitter/combiner to the input of the spectrum analyzer with an SMA cable.
 - (d) Connect the output ports of the two synthesizers (labeled “RF Out”) with the output ports of splitter/combiner (labeled “1” and “2”) via male-male SMA adapters. Fig. 17 shows the measurement setup.
 - (e) Preset the spectrum analyzer and configure it as below.
 - i. Center frequency = 2.4 GHz;
 - ii. Span = 20 MHz;
 - iii. RBW = 100 kHz;
 - iv. Reference level = 20 dBm.
 - (f) Launch another instance of the SynthMachine software (now you should have two instances of SynthMachine running) and choose the appropriate calibration file (serial number) for the second TPI synthesizer. Set the “Center Frequency” to 2400 MHz for the first synthesizer and 2401 MHz for the second. Set the “Output Power” to 10 dBm for both synthesizers.

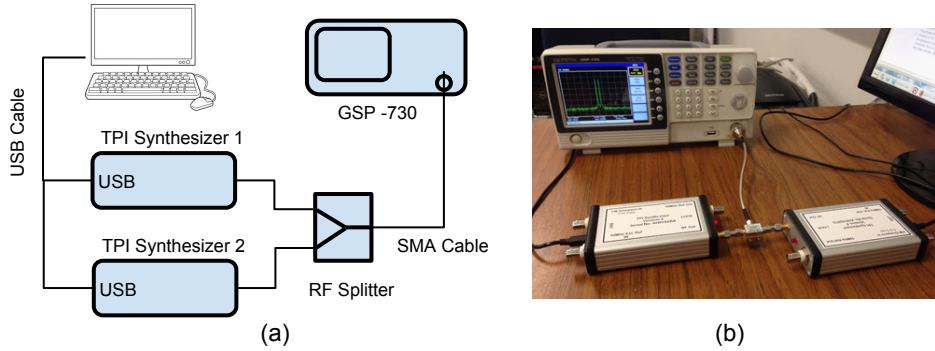


Figure 17: Two-tone measurement setup.

- (g) Now turn on the TPI synthesizers by clicking the “RF On” buttons in both instances of the SynthMachine software.
- (h) The screen of the spectrum analyzer should look similar to Fig. 18.

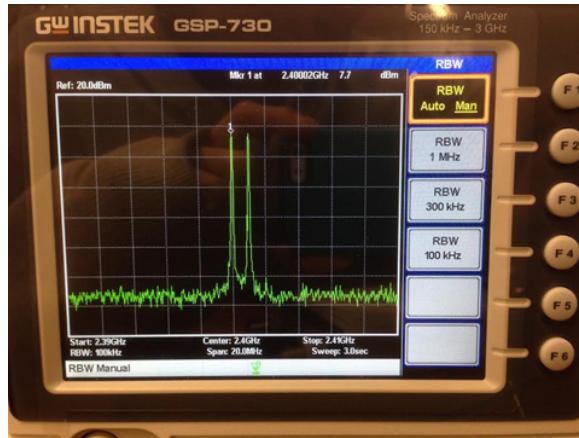


Figure 18: Screenshot of the spectrum analyzer with two-tone input.

- (i) Set the RBW to the three possible manual options. Capture the screen for each of the three settings. Describe the differences between the three screen captures and explain why such differences exist in your lab report.

5.2 Characterizing the bandwidth and the gain

1. Connect the output port of LNA (labeled “OUT”) to one end of a 3-dB attenuator¹¹, then connect the other end of the attenuator to the spectrum analyzer with an SMA cable.

¹¹The use of an attenuator here is to limit the RF power input to the spectrum analyzer for more accurate result. This should not be necessary on a better spectrum analyzer.

2. Connect the input port of the LNA to the TPI synthesizer via a SMA male-to-male connector.

Note: In general, always terminate the input and output ports of an RF amplifier before applying dc power.

3. Connect the “+5VDC” pin of the amplifier to the positive terminal of the lab power supply using a wire; connect the “GND” pin of the amplifier to the ground of the power supply. Fig. 19 shows the measurement setup.

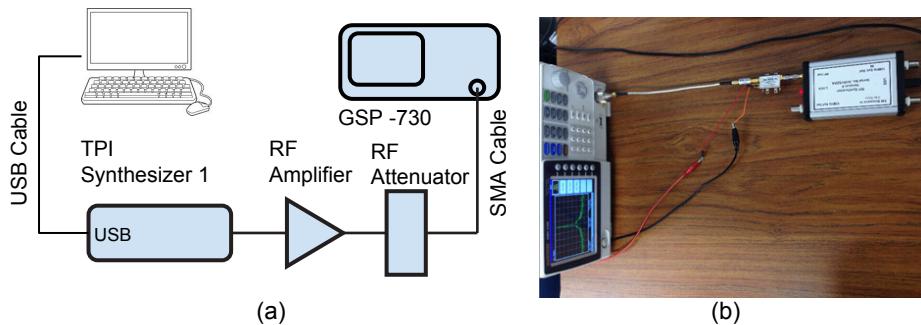


Figure 19: Amplifier bandwidth and gain measurement setup.

4. Preset the spectrum analyzer and configure it as below.
 - (a) Center frequency = 2.4 GHz;
 - (b) Span = 4 MHz;
 - (c) Reference level = -10 dBm;
 - (d) RBW = auto.
5. Configure the TPI synthesizer as follows:
 - (a) Center Frequency = 2.4 GHz;
 - (b) Output Power p_{out} = -25 dBm.
6. Set the power supply to output +5 V.
7. Verify that the amplifier is drawing approximately 55 mA of dc current. This indicates—to some extent—that the amplifier is working well and is not damaged.
8. Turn on the TPI synthesizer.
9. You should now see a signal at 2.4 GHz on the spectrum analyzer.
10. Press the “Peak Search” button on the spectrum analyzer, and a marker is automatically located at the desired signal. Let P_{meas} be the measured signal power.

11. Calculate the gain of the amplifier.

$$G = P_{meas} - P_{out} - (P_{cal} - 10) + 3 \quad (\text{dB}).$$

Verify that this value agrees with the amplifier's datasheet. Explain why the above equation is used to calculate the gain.

12. Now sweep set the output frequency of the TPI synthesizer from 2.0 GHz to 3.0 GHz (include at least 8 data points) and measure the amplifier gain at each frequency. Note each time when you are changing the output frequency of TPI synthesizer, you also need to change the center frequency of spectrum analyzer, otherwise you won't observe any signals. Please note down the frequency and the measured power, then use the above formula to calculate the gain. Plot the gain with respect to frequency. Include at least 8 data points. What is the 3 dB bandwidth of the amplifier? What is the maximum gain variation in the 2.3–2.7 GHz range? Does the measured data agree well with the datasheet?

5.3 Measuring P_{1dB}

Using the same setup as in Experiment 5.2, we will measure the 1-dB compression point of the amplifier.

1. Preset and configure the spectrum analyzer as follows:
 - (a) Center frequency = 2.4 GHz;
 - (b) Span = 4 MHz;
 - (c) RBW = auto;
 - (d) Reference level = -10 dBm.
2. Set the synthesizer output frequency to 2.4 GHz.
3. Set the output power of the TPI synthesizer from -20 dBm to 10 dBm in steps of 1 dBm. Record the measured signal power (output of the amplifier) on the spectrum analyzer. Note when you increase the input power to some extent, the signal peak will be out of screen range, but you can always find the peak value by pressing the "Peak Search" button on the spectrum analyzer. Though you can adjust the reference level to a higher value to observe the signal peak, this change would lead to a poor measurement result.
4. Plot the measured output power vs. the input power. What is the output 1 dB compression point for the amplifier? Does it agree with the datasheet?

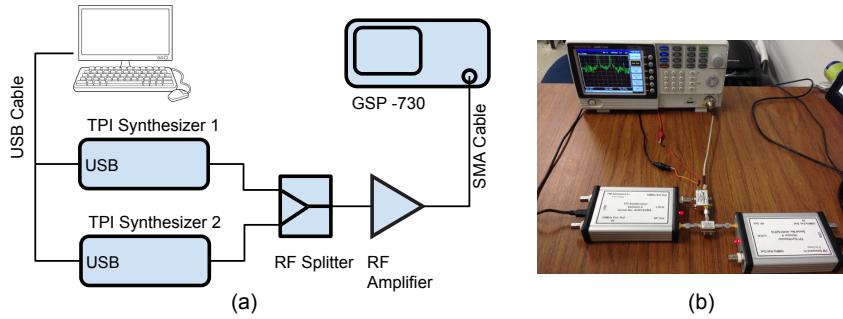


Figure 20: Amplifier IP3 measurement setup.

5.4 Measuring IP3

1. For the IP3 measurement, we need two input signals with a slight frequency offset. Set up the measurement as illustrated by Fig. 20.
2. Preset and configure the spectrum analyzer as follows:
 - (a) Center frequency = 2.4005 GHz;
 - (b) Span = 4 MHz;
 - (c) RBW = auto
 - (d) Reference level = -20 dBm.
3. Configure the TPI synthesizers as follows:
 - (a) Synthesizer 1:
 - i. Output frequency = 2.4 GHz;
 - ii. Output power = -10 dBm;
 - (b) Synthesizer 2:
 - i. Output frequency = 2.401 GHz;
 - ii. Output power = -10 dBm.
4. The spectrum analyzer screen should look like the following. The fundamental signals will be beyond what the screen can display (Fig. 21-b); we do this intentionally to keep the reference level small (-20 dBm) to obtain a better measurement result. You can use "F1" - "F6" key to locate every fundamental tone and 3rd order intermodulation (IM3) signals.
5. Sweep the output power of both TPI synthesizers from -25 dBm to 5 dBm. Record the measured fundamental and IM3 signal power. The two IM3 signals may exhibit different power levels. This may be caused by a number of reasons, such as gain variation and memory nonlinear effects. For this lab, simply pick one of the two IM3 signals.
6. Plot the measured fundamental and IM3 signal power vs. the input power. What is the output IP3 (OIP3) point for the amplifier? Does it agree with the datasheet?

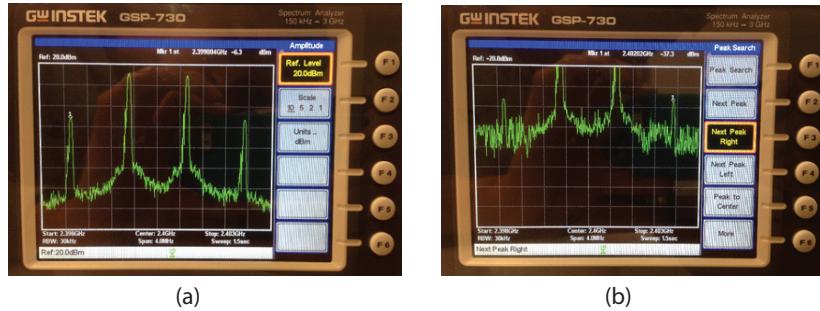


Figure 21: Screenshot of the amplifier two-tone measurement. (a) Low signal level; (b) High signal level.

5.5 RF PCB designs

5.5.1 RF Amplifier PCB

Design a test PCB for the ADI ADL5611 RF gain block IC. Before you start your design, it would be helpful to go through Example 2 of the EEC 134 PCB Design Tutorial.

1. Follow the recommended schematic and layout in the datasheet: (http://www.analog.com/static/imported-files/data_sheets/ADL5611.pdf). Your final circuit will look similar, but may not be identical to the ADL5611 evaluation board (Fig. 22).

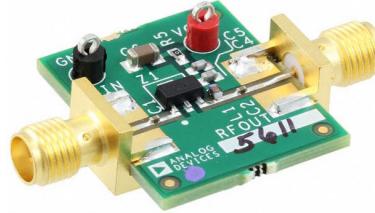


Figure 22: Evaluation board for ADI ADL5611.

2. Use Bay Area Circuits as the PCB vendor. Your PCB design should conform to the Bay Area Circuits student specials specifications.
3. The PCB area should not exceed $1 \times 1 \text{ in}^2$.
4. Make sure that you have 50Ω transmission lines for the input and output SMA connectors.
5. The recommended footprint of the SMA connectors are available at this link. It is also available in the “resources” folder.
6. Use 0603 sized SMD resistors and capacitors.

7. The TA will provide the ADL5611 IC and SMA connectors. You will be responsible for acquiring the rest of the circuit components. Do remember to check the class inventory.
8. The following items are due by **Oct. 30th, 2015**. Refer to Table. 1 for submission instructions.
 - A PCB design report to the TA. The design report should include the following:
 - Bill of materials.
 - Screen capture of the schematic.
 - Screen capture of the PCB layout.
 - Bay Area Circuit design for manufacturing (DFM) report from showing no errors.
 - A PCB review report to the TA. The review report should be completed by a different team than yours. You will be responsible for finding this review team. The review report should follow the general guideline of the PCB Review Report Template.
 - PCB output (Gerber) files.
9. After the PCB comes back, you will need to assemble the circuit and test it. The tests would be similar to what you have done in Measurement 5.1–5.4. Test report for this PCB is due by **Nov. 20th, 2015**.

5.5.2 RF variable attenuator PCB

Design a test PCB for the Skyworks SKY12322-86LF variable attenuator.

1. Follow the recommended schematic (Fig. 8) in the datasheet:
(<http://www.skyworksinc.com/uploads/documents/200218C.pdf>).
Fig. 7 of the datasheet shows the layout of the SKY12322-86LF evaluation board. However, your PCB design doesn't need to be this big.
2. The PCB area should not exceed 1 in \times 1 in.
3. You should use your Teensy micro-controller for setting the attenuation level. Note that the Teensy digital pins have internal pull-up resistors.
4. Use Bay Area Circuits as the PCB vendor. Your PCB design should conform to the Bay Area Circuits student specials specifications.
5. Make sure that you have 50Ω transmission lines for the input and output SMA connectors.
6. The TA will provide the SKY12322-86LF IC and SMA connectors. You will be responsible for acquiring the rest of the circuit components. Do remember to check the class inventory.

7. The following items are due by **Nov. 6th, 2015**. Refer to Table. 1 for submission instructions.
 - A PCB design report to the TA. The design report should include the following:
 - Bill of materials.
 - Screen capture of the schematic.
 - Screen capture of the PCB layout.
 - Bay Area Circuit design for manufacturing (DFM) report showing no errors.
 - A PCB review report to the TA. The review report should be completed by a different team than yours. You will be responsible for finding this review team. The review report should follow the general guideline of the PCB Review Report Template.
 - PCB output (Gerber) files.
8. After the PCB comes back, you will need to assemble the circuit and test it. The main test is the attenuation level at various attenuation settings. Test report for this PCB is due by **Nov. 27th, 2015**.

References

- [1] Jeff Thomas, Tom Holmes, Terri Hightower, “Learn RF Spectrum Analysis Basics,” Agilent Technologies, <https://www.jlab.org/uspas11/Reading/RF/RF%20Spectrum%20Analysis.pdf>.
- [2] Erik Diez, “The Fundamentals of Spectrum Analysis,” Agilent Technologies, <http://electronicdesign.com/test-amp-measurement/fundamentals-spectrum-analysis>.